

Reg. No. _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
FIRST SEMESTER REGULAR MCA DEGREE EXAMINATION, DEC 2016

Course Code: RLMCA109
Course Name: DIGITAL FUNDAMENTALS

Max. Marks: 60

Duration: 3 Hours

PART A

Answer All Questions
Each question carries 3 marks

1. Perform the following binary operations using the given unsigned numbers.
 - a. $11011100.011 + 100111.11$
 - b. $11101 \div 101$
2. Simplify the Boolean expression $(\overline{A} \overline{B} \overline{C}) + (\overline{A} \overline{B} C)$
3. Which gates are called universal gates? Why it is called so?
4. What is a demultiplexer? Discuss the differences between a demultiplexer and a decoder.
5. What is parity generator and checker?
6. What is a Flip Flop? Why is it called a bistable multivibrator?
7. What is a register?
8. What is a shift register? Can a shift register be used as a counter? If Yes how?

PART B

Answer any one question from each module. Each question carries 6 marks

9. How can you represent single precision floating point numbers? Give example.

Or

10. Represent the following decimal numbers in 8bit 1's complement and 8bit 2's complement form.
 - i. 24
 - ii. -90
 - iv. 100(3 x 2)
11. Minimize the following logic function using K-maps and realize using two input NAND gates.

$$F(A,B,C,D) = \sum m(1,3,5,8,9,11,15) + d(2,13)$$

E C1E004

Or

12. A combinational circuit has 3 inputs A, B, C and output F.

F is true for following input combinations

A is False, B is True

A is False, C is True

A, B, C are False

A, B, C are True

(i) Write the Truth table for F. Use the convention True=1 and False = 0.

(ii) Write the simplified expression for F in SOP form.

(iii) Draw logic circuit using minimum number of two input gates. (3x2)

13. What is a full adder? Draw the block diagram and explain the working of a binary adder, which can be used to add two 4-bit binary numbers.

Or

14. Implement the three variable function given by $F(A, B, C) = \sum m(1, 3, 5, 6)$ using a Multiplexer

15. Convert RS flip flop to JK flip flop and draw the block diagram

Or

16. Draw the diagram of a Master-slave J-K flip-flop. What is race around condition? How is it eliminated in a Master-slave J-K flip flop?

17. Design a mod-12 Synchronous up counter

Or

18. Using D-Flip flops and waveforms explain the working of a 4-bit SISO shift register.

19. Draw the block diagram and explain the basic component of a PC

Or

20. What is Raspberry Pi? Explain the architecture of Raspberry.